# Benha University Faculty of Engineering at Shoubra Electrical Engineering Department 1st Year Communications



Final Term Exam
Date: Tuesday 24/5/2016

**Subject: Test (1) Duration: 2 hours** 

No. of questions : 2 (In part I)

• Total Mark: 50 Marks

#### Answer all the following questions

#### · Illustrate your answers with sketches when necessary

### Part I [25 Marks]

## Question (1)[12 marks]


- A. Explain how you can calculate [4 marks]:
  - Capacitors in parallel and series.

$$Cs = (1/C1 + 1/C2 + ...)^{-1}$$
  
 $Cp = (C1 + C2 + ...)$ 

• Inductors in parallel and series.

Lp = 
$$(1/L1 + 1/L2 + ...)^{-1}$$
  
Ls =  $(L1 + L2 + ...)$ 

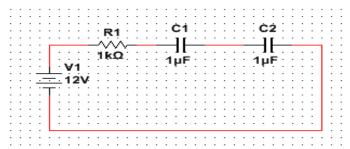- B. For the following figure find: [8 marks].
  - The equivalent capacitance.
  - The time constant.



$$Ceq = C1*C2 / C1+C2$$
  
= 0.5 UF


Time Constant = Ceq \* R = 1K \*0.5 UF = 0.5 m Sec

## Question (2)[13 marks]


- A. Explain the relation between I and V for [6 marks]:
  - Pure R.




• Pure L.

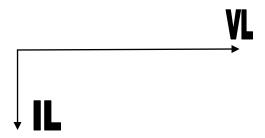

• R and L.

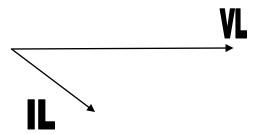

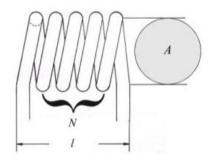B. Explain how you can compute the inductance of the coil shown below. [7 marks]




**Answer** 

Winding a conductor into successive loops results in a coil through which magnetic field lines pass when the coil conducts a current. The magnetic field's intensity is characterized by the magnetic flux. Changes in the magnetic flux through the coil (due to changes in amperage, for example) give rise to a self-induced voltage in the coil; this voltage's value depends on the current's rate of change, and on the coil's size and nature. The coil's inductance L is a measure of its ability to generate self-induced voltages. The following relationship applies to an elongated coil:

$$L = \mu_0 \cdot \mu_{\mathbf{r}} \cdot \frac{N^2}{l} \cdot A$$

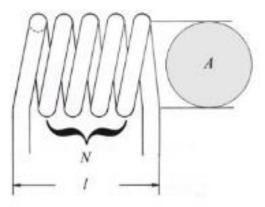 $\mu_0$  is the magnetic field constant,  $\mu_r$  the coil core's relative permeability, N the number of windings, I the coil's length, and A the coil's cross-section (see the diagram below).



The unit of inductance is the *Henry* (symbol H, 1 H = 1 Vs/A). A coil has an inductance of 1 H if a uniform change of 1 A per second in the coil current induces a voltage of 1 V.

GOOD LUCK DR .MICHAEL NASIEF