



- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- The exam consists of **Two** pages
- Total Mark: **75** Marks
- Examiners: Dr. Moataz Elsherbini
- **(put your final results in a border)**

**1<sup>st</sup> paper**

**1.**

(a) It is required to broadcast a **shoubra radio** station to be detected through your FM radio. Design a suitable series RLC circuit to verify this mission. The station must be heard within bandwidth of 2MHz, while the most purity sound heard at 90MHz. **(6 marks)**

(b) Another friend of your project team claimed that he can use passive BPF (using Resistors and Capacitors only) to achieve the same resonant frequency and bandwidth. Help him reaching the suitable design. **(6 marks)**

(c) Another friend of your project team claimed that he can use passive BPF (using Resistors and Capacitors only) to achieve the same resonant frequency and bandwidth. Help him reaching the suitable design. **(6 marks)**


(d) A genius student tries to change the design to obtain Quality factor of 55 at BW of 2MH. will he success receiving the channel with FM mobile radio?(why?) **(2 marks)**

**2.**

(a) for the circuit shown in figure (1), use (d/dt instead of  $j\omega$ ) to determine


$V_1$  if  $i_2 = 4\sin 38t$  and  $i_1 = 0$ ;

$V_2$  if  $i_1 = -5e^{-2t}$  and  $i_2 = 0$ .

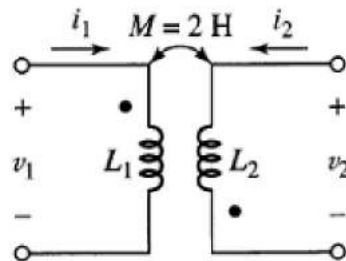

**Figure (1) (8 marks)**

(b) for the following fixed power supply circuit shown in figure (2), calculate the secondary voltage and the turns ratio of the transformer, if pin(1) of the IC regulator reads a voltage greater than the DC output by 3.57V.

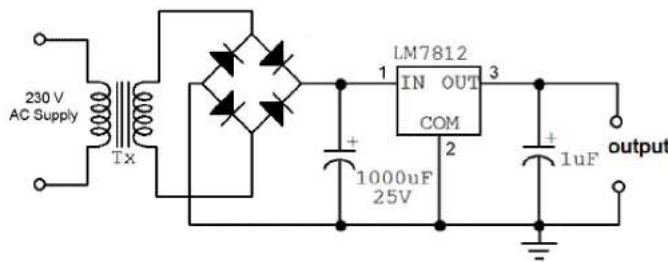

**Figure (2) (7 marks)**



2<sup>nd</sup> paper

3.

(a) Write KVL equations for the two loops of the following magnetically coupled circuit

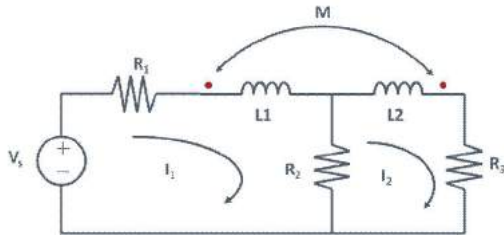


Figure (3) (8 marks)

(b) In the circuit of Figure (4), Find the mathematical expression for  $i_c(t)$  and  $V_c(t)$ .

- switch is closed on position 1 at  $t=0$ .
- switch is closed on position 2 at  $t=40$  msec.
- switch is closed on position 3 at  $t=60$  msec.

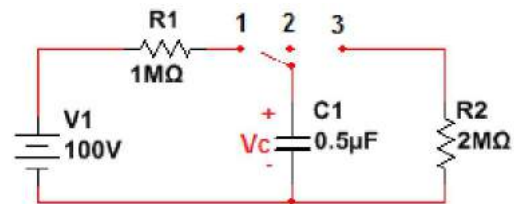


Figure (4) (12 marks)

4.

(a) If  $(V_s / R)$  shown in figure (5) is DC current source; Using laplace; Extract the mathematical expressions for the instantaneous current and Voltage of the capacitor and resistor if the Switch (s) closed at  $t=0$ .

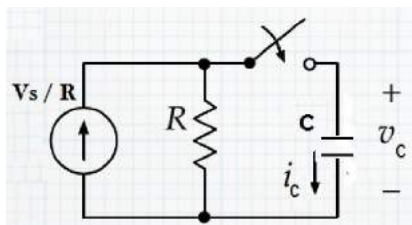


Figure (5) (12 marks)

(b) A three phase star-connected system having a phase voltage of 230V and loads consist of non reactive resistance of 4 Ω, 5 Ω and 6 Ω respectively. Calculate:

- (i) the current in each phase conductor
- (ii) the current in neutral conductor
- (iii) total power absorbed (8 marks)

- 1 -

①  $f_0 = 90 \text{ MHz}$ ,  $BW = 2 \text{ MHz}$ , Series RLC resonance

Sol/ 08  $BW = \frac{R}{L}$  (rad/sec)

$$\therefore (2 \times 10^6 \times 2\pi) = \frac{R}{L}$$

Let  $R = 100 \Omega$   $\therefore L = \frac{100}{2 \times 10^6 \times 2\pi} \approx 7.95 \mu\text{H}$

$\therefore \omega = \frac{1}{\sqrt{LC}} \therefore 2\pi \times 90 \times 10^6 = \frac{1}{\sqrt{7.95 \times 10^{-6} \times C}}$

$\therefore C \approx 0.39 \text{ pF}$

$Q = \frac{f_0}{BW} = \frac{90 \text{ M}}{2 \text{ M}} = 45$

جواب

$Q = \frac{\omega L}{R} = \frac{1}{\omega RC}$

$\omega = 2\pi \times 90 \times 10^6$   
 $\therefore 45 = \frac{(2\pi \times 90 \times 10^6) L}{R}$

Let  $R = 100$ ,  $L = 7.95 \mu\text{H}$

$45 = \frac{1}{(2\pi \times 90 \times 10^6) \times 100 \times C} \therefore C = 0.39 \text{ pF}$

## ② ideal parallel Res

- 2 -

$$Q = 45 = \frac{R}{\omega L} = \omega RC$$

$$BW = \frac{1}{RC}$$

مثال ١

$$BW = \frac{1}{RC} \text{ rad/sec}$$

$$2\pi \times 2 \times 10^6 = \frac{1}{RC}$$

فيكون  $R$  و  $C$  في  $\parallel$   
 (في الحقيقة  $\parallel$  فقط)

2/ You select  $R = 100 \Omega$

$$C_1 = \frac{1}{2\pi \times 2 \times 10^6 \times 100} = 0.795 \text{ nF}$$

3/ You select  $R = 1 \text{ k}$

$$C_2 = 79.5 \text{ pF}$$

$$\omega = \frac{1}{\sqrt{LC_1}} = 2\pi \times 90 \times 10^6$$

$$L_1 = 3.93 \text{ nH} \quad R = 100 \Omega$$

4/ used  $C_2$   $1 \text{ k} \approx R$  فيكون

$$L_2 = 39.3 \text{ nH}$$

مثال ٢

$$Q = \omega RC \text{ at } (R = 100 \Omega)$$

$$45 = (2\pi \times 90 \times 10^6)(100)C = 45$$

$$\therefore C = 0.795 \text{ nF}$$

$$\text{at } R = 1 \text{ k} \quad C = 79.5 \text{ pF}$$



$$Q = \frac{R}{\omega L}$$

$$45 = \frac{100 \text{ (or } 1000)}{(2\pi \times 90 \times 10^6)L}$$

$$\begin{array}{l} \swarrow \quad \searrow \\ R = 100 \quad R = 1000 \\ L = 3.93 \text{ nH} \quad L = 39.3 \text{ nH} \end{array}$$

∴  $\omega = 710$  ∴  $f_1 = f_0 - BW/2 = 90 - \frac{1}{2} = 89.5 \text{ MHz}$   
 use Approx.  $f_2 = f_0 + BW/2 = 90.5 \text{ MHz}$

③ BPF using  $R^1LC^1$

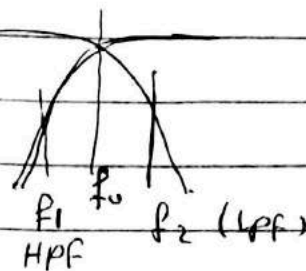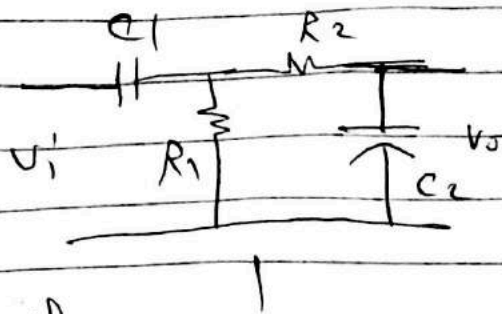

$$f_1 = \frac{1}{2\pi R_1 C_1}$$

$$f_1 = f_0 - BW/2 = 89 \text{ MHz}$$

HPF  $\Rightarrow 89 \times 10^6 = \frac{1}{2\pi (100) C_1}$  let  $R_1 = 100$

$$C_1 = 56.1 \text{ pF}$$

$$f_2 = \frac{1}{2\pi R_2 C_2}$$

LPF  $f_2 = f_0 + BW/2 = 91 \text{ MHz}$

$$91 \text{ MHz} = \frac{1}{2\pi (100) C_2} \quad \text{let } R_1 = R_2$$

$$C_2 = 54.9 \text{ pF}$$

④  $Q = 55, BW = 2 \text{ MHz}$

$$\therefore Q = f_0/BW, \quad f_0 = 2 \times 55 \text{ MHz} = 110 \text{ MHz}$$

$$\therefore 2710, \quad f_1 = f_0 - BW/2 = 109 \text{ MHz}$$

$$f_2 = f_0 + BW/2 = 111 \text{ MHz}$$

$\therefore f_0, f_1, f_2$  out of range of FM Band

where FM Band is between 88M & 108 MHz

Will not Relieve

Q (2) \*

①

①  $O/p = 12V$

$$V_{pin1} = 12 + 3.57 = 15.57V$$

$$V_{sec} = V_{pin} + 1.4 = 16.97V$$

$\swarrow$   $V_{Diode}$        $\searrow$   $V_{max}$

$$\therefore V_{secrms} = \frac{16.97}{\sqrt{2}} \approx 11.997 \approx 12V_{rms}$$

$$\text{turn ratio} = \frac{280}{12} = 19.16 \approx 19$$

②  $V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$

at  $V_1$ ,  $i_1 = 0$ ,  $i_2 = 4 \sin 38t$

$$\therefore V_1 = 0 - 2 \times \frac{d(4 \sin 38t)}{dt} = -2 \times 4 \times 38 \cos 38t$$

$$= -304 \cos 38t$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = -2 \times \frac{d(-5e^{-2t})}{dt} = -2 \times -5 \times -2e^{-2t}$$

$$= -20e^{-2t}$$



## Q (3-a)

$$\text{KVL } I_1 : (R_1 + R_2 + j\omega L_1)I_1 - j\omega M I_2 - R_2 I_2 = V_s \dots\dots\dots (1)$$

$$\text{KVL } I_2 : -R_2 I_1 + (R_2 + R_3 + j\omega L_2)I_2 - j\omega M I_1 = 0 \dots\dots\dots (2)$$

## Q(3-b)

(12 Marks)

3-b at S at Pos (1)

$$V_c(t) = V - V e^{-t/\tau} = 100 \left( 1 - e^{-\frac{t}{1 \times 10^{-6} \times 0.5 \times 10^{-6}}} \right) =$$

$$V_c(t) = 100 (1 - e^{-2t})$$

$$i_c(t) = C \frac{dV_c(t)}{dt} = 0.5 \times 10^{-6} \times 100 \times 2 \times e^{-2t} = 100 e^{-2t}$$

at  $t = 40 \mu s$   $V_c = 7.68 V$   $i_c = 1 \times 10^{-4} A$

at Pos (2)  $V_c = 7.68$   
 $i_c = 1 \times 10^{-4}$

at Pos (3)  $V_c(t) = 7.68 e^{-t/(2 \times 0.5)} = 7.68 e^{-t}$

$$i_c(t) = C \frac{dV_c(t)}{dt} = 0.5 \times 10^{-6} \times 7.68 (-1) e^{-t} = -3.84 e^{-t-6}$$

# Q (4-a)

- Assume the switch S is closed at  $t = 0$
- Apply KVL to the series RC circuit shown:

$$\left[ \frac{1}{c} \int i(t).dt + v_c(0) \right] + R.i(t) = V$$

- Apply Laplace Transform on both sides

$$\left[ \frac{I(s)}{cs} + \frac{v_c(0)}{s} \right] + R.I(s) = \frac{V}{s}$$

$V_c(0) = 0 \gg$  initial value of the voltage at  $t = 0$


$$I(s).[R + \frac{1}{cs}] = \frac{V}{s}$$

$$I(s) = \frac{V/s}{[R + 1/cs]} = \frac{V/R}{[s + 1/cR]}$$

- Apply the inverse Laplace Transform technique to get the expression of the current  $i(t)$

$$i(t) = \frac{V}{R} e^{-\frac{1}{RC}t}; t > 0$$

The same as last lecture

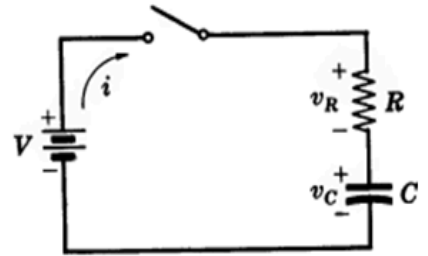


# Q(4-b)


$$I_{4\Omega} = \frac{230}{4} = 57.5A$$

$$I_{5\Omega} = \frac{230}{5} = 46A$$

$$I_{6\Omega} = \frac{230}{6} = 38.3A$$

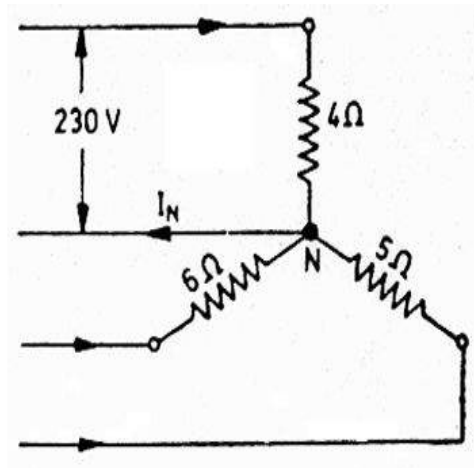



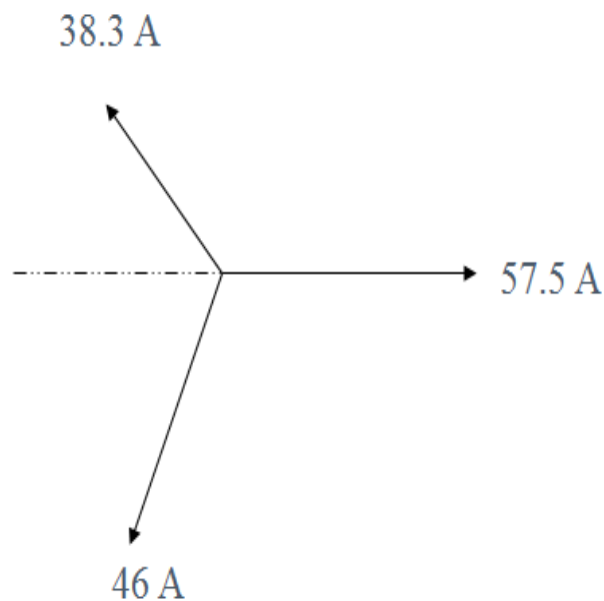

(b)

$$\text{X-component} = -46 \sin 30^\circ - 38.3 \sin 30^\circ + 57.5 = -15.35 \text{ A}$$

$$\text{Y-component} = -46 \cos 30^\circ + 38.3 \cos 30^\circ = -6.67 \text{ A}$$

Therefore  $I_N = \sqrt{15.35^2 + 6.67^2} = 16.7 \text{ A}$

(c)  $P = 230(57.5 + 46 + 38.3) = 32.61 \text{ kW}$