



- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- The exam consists of **Two** pages
- Total Mark: **75** Marks
- Examiners: Dr. Moataz Elsherbini
- **(put your final results in a border)**

1st paper

1. It is required to broadcast a **shoubra radio** station which detected through FM radio. Design a suitable practical parallel resonance circuit using coil has impedance of $10 + j3000\Omega$ to verify the required broadcasting. The circuit has to be heard between (89MHz and 91 MHz) and very clear at 90MHz. **Don't use any approximations. (10 marks)**

2. (a) Calculate the transfer function and determine the type of filter shown in Figure (1)

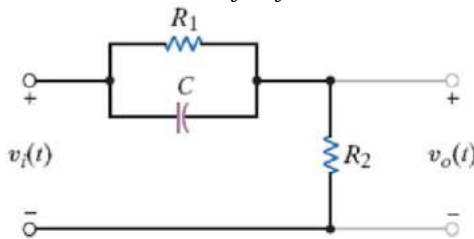


Figure (1) (8 marks)

(b) Calculate phasor currents I_1 and I_2 in the circuit of Figure (2).

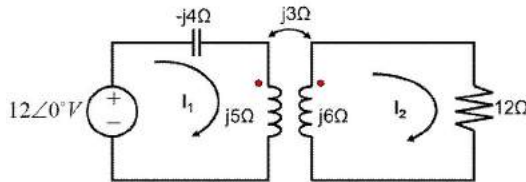


Figure (2) (7 marks)

3. (a) Write KVL equations for the two loops of the following magnetically coupled circuit

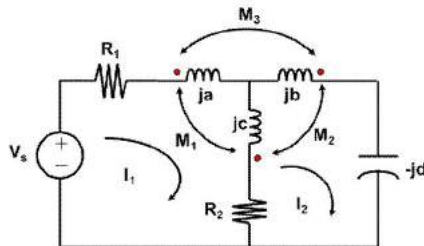


Figure (3) (8 marks)

(b) In the circuit of Figure (4), Find the mathematical expression for $i_c(t)$ and $V_c(t)$.

- switch is closed on position 1 at $t=0$.
- switch is closed on position 2 at $t=40$ msec.
- switch is closed on position 3 at $t=60$ msec.

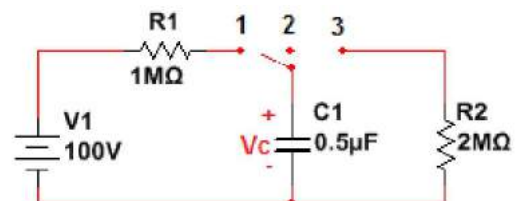


Figure (4) (12 marks)



2nd paper

4. If (V_S / R) shown in figure (5) is DC current source; Using laplace; Extract the mathematical expressions for the instantaneous current and Voltage of the inductor and resistor if the Switch (s) closed at $t=0$.

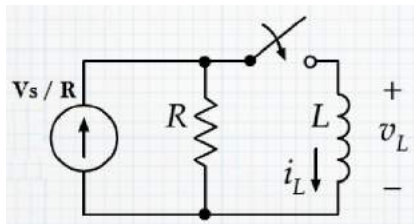


Figure (5) (12 marks)

5. (a) A three phase star-connected system having a phase voltage of 230V and loads consist of non reactive resistances of 4 Ω , 5 Ω and 6 Ω respectively. Calculate:

- (i) the current in each phase conductor
- (ii) the current in neutral conductor
- (iii) total power absorbed (12 marks)

- (b) For the Common emitter circuit in figure (7), if the measured voltage between base and emitter was 0.73V, $\beta=200$, calculate :

$$(I_B / I_C / V_C / V_E / V_B / V_{CE})$$

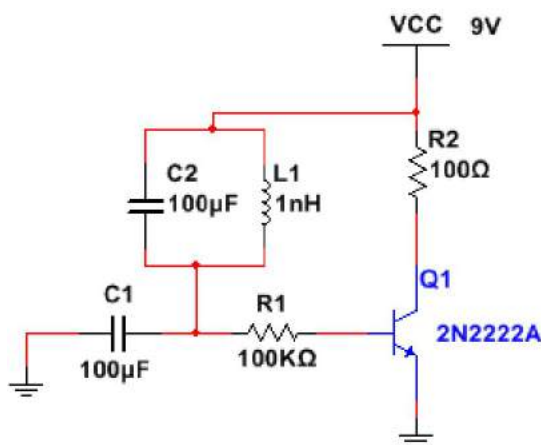


Figure (7) (6 marks)

Model answer

Final

10 Marks

①


$$L = R_{eL} + jX_L = 10 + j3000$$

$\swarrow \quad \searrow$
 $R_e \quad X_L$


$$f_0 = 90 \text{ MHz}$$

$$BW = 2 \text{ MHz} \quad \begin{matrix} > f_1 = 89 \text{ MHz} \\ > f_2 = 91 \text{ MHz} \end{matrix}$$

Design practical parallel

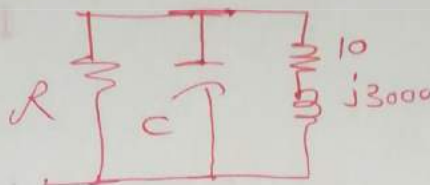

Convert to ideal

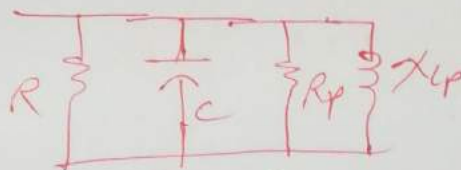

$$R_p = \frac{R_e^2 + X_L^2}{R_e} = \frac{10^2 + 3000^2}{10} \approx 900 \text{ k}$$

$$X_{Lp} = \frac{R_e^2 + X_L^2}{X_L} = \frac{10^2 + 3000^2}{3000} \approx 3000$$

$$Q = \frac{f_0}{BW} = \frac{90}{2} = 45$$

$$\omega_p = 2\pi f_p = 2\pi \times 90 \text{ MHz} = 565.4 \text{ Mrad/s}$$

$$Q = \frac{X_{Lp}}{R_p} = 45 \quad \therefore R_p = \frac{3000 \times 45}{45} = 135 \text{ k}$$

$$\frac{1}{135 \text{ k}} = \frac{1}{900 \text{ k}} + \frac{1}{R_1}$$


$$R_1 = \frac{135 \times 900}{135 - 90} = 158.82 \text{ k}$$

$$BW = \frac{1}{RC} = 2 \times 10^6 \times 2 \times \pi$$

$\swarrow \quad \searrow$
 $R \quad C$
 $158.82 \text{ k} \quad 3000$

$$C \approx 0.25 \text{ pF}$$

2-a 8 Marks

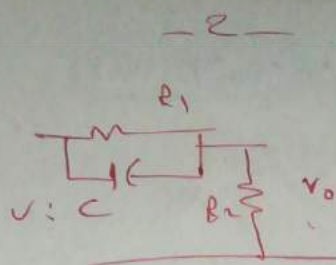

$$Z_1 = \frac{R_1 \left(\frac{1}{j\omega C} \right)}{R_1 + \frac{1}{j\omega C}} = \frac{R_1}{1 + j\omega R_1 C}$$

$$\frac{V_o}{V_i} = \frac{R_2}{R_2 + \frac{R_1}{1 + j\omega R_1 C}} = \frac{(1 + j\omega R_1 C) R_2}{R_1 + (1 + j\omega R_1 C) R_2}$$

$$\text{at } \omega = 0 \rightarrow \frac{V_o}{V_i} = 0$$

$$\text{at } \omega = \infty \rightarrow \frac{V_o}{V_i} = 1$$



hpf

2-b

$$-12 + (-j4 + j5)I_1 - j3I_2 = 0$$

$$jI_1 - j3I_2 = 12 \rightarrow (1)$$

$$-j3I_2 + (12 + j6)I_2 = 0$$

$$I_1 = \frac{(12 + j6)I_2}{j3} = (2 - j4)I_2 \rightarrow (2)$$

$$\text{solve (1) \& (2)} \quad I_2 = \frac{12}{4 - j} = 2.91 \angle 14.04^\circ \text{ A}$$

$$I_1 = (2 - j4)I_2 = 13.01 \angle -49.39^\circ \text{ A}$$

7 marks

3-a 8 marks

$$V_s = I_1(R_1 + j\omega L_1 + j\omega L_2 + R_2) - I_2(j\omega L_2 + R_2) - j\omega M_1(I_1 - I_2) + j\omega M_2 I_2 - j\omega M_3 I_2$$

$$0 = I_2(R_2 + j\omega L_2 + j\omega L_3 - j\omega L_1) - I_1(j\omega L_2 + R_2) - j\omega M_2(I_2 - I_1) - j\omega M_3 I_1 + j\omega M_1 I_1$$

(12 Marks)

3-b at S at Pos (1)

$$V_c(t) = V - V e^{-t/\tau} = 100(1 - e^{-\frac{t}{1 \times 10^{-6} \times 0.5 \times 10^{-6}}}) =$$

$$V_c(t) = 100(1 - e^{-2t})$$

$$i_c(t) = C \frac{dV_c(t)}{dt} = 0.5 \times 10^{-6} \times 100 \times 2 \times e^{-2t} = 100 e^{-2t}$$

at $t = 40 \mu s$ $V_c = 7.68V$ $i_c = 1 \times 10^{-4} A$ دالة الجهد

at Pos (2) $V_c = 7.68V$ $i_c = 1 \times 10^{-4} A$ معدل الجهد


at Pos (3) $V_c(t) = 7.68 e^{-\frac{t}{1 \times 10^{-6} \times 0.5 \times 10^{-6}}} = 7.68 e^{-t}$

$$i_c(t) = C \frac{dV_c(t)}{dt} = 0.5 \times 10^{-6} \times 7.68 (-1) e^{-t} = -3.84 e^{-t}$$



Q(4) (12 Marks)

v, v at L, R
Laplace

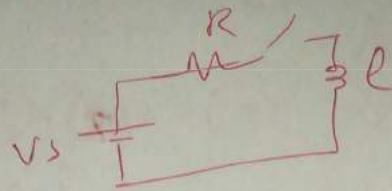

$$Ri + L \frac{di}{dt} = V$$

$$R I(s) + L (s I(s) - i(0)) = V/s$$

$$\therefore I(s) (R + sL) = V/s$$

$$\therefore I(s) = \frac{V}{s(R + sL)} = \frac{N/L}{s(s + R/L)} = \frac{A_1}{s} + \frac{A_2}{(s + R/L)}$$

$$\therefore I(s) = \frac{A_1(s + R/L) + A_2(s)}{s(s + R/L)} = \frac{N/L}{s(s + R/L)}$$

$$\therefore N/L = A_1 R/L \quad \therefore A_1 = N/R$$

$$\therefore A_2 s + A_1 R/L = 0 \quad \therefore A_2 = -A_1 = -N/R$$

$$\therefore I(s) = \frac{N/R}{s} - \frac{N/R}{s + R/L}$$

$$\therefore i(t) = N/R (1 - e^{-R/L t})$$

$$i(t) = N/R (1 - e^{-R/L t})$$



$$V_R = i(t) \times R = N (1 - e^{-R/L t})$$

$$V_C = V - V_R = N - N (1 - e^{-R/L t})$$

$$= N e^{-R/L t}$$

Q 5-a) 12 Marks

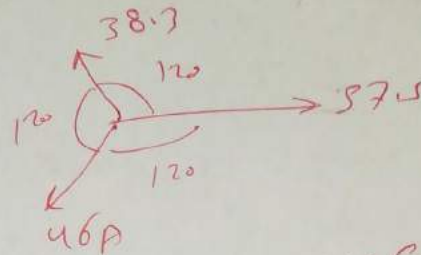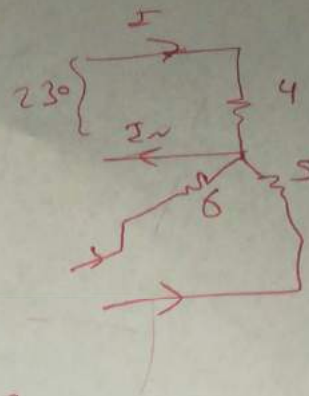a) $I_4 = \frac{230}{4} = 57.5 \text{ A}$
 $I_5 = \frac{230}{5} = 46 \text{ A}$
 $I_6 = \frac{230}{6} = 38.3 \text{ A}$



b) $X_{\text{comp}} = 57.5 - 38.3 \cos 30 - 46 \cos 30 = -15.5 \text{ A}$
 $Y_{\text{comp}} = 38.3 \sin 30 - 46 \sin 30 = -3.9 \text{ A}$
 $I_N = \sqrt{(-15.5)^2 + (-3.9)^2} = 16 \text{ A}$

c) $P = 230 (57.5 + 46 + 38.3) = 32.61 \text{ kW}$